

Circuits Theory and Electronic Fundamentals

Integrated Master in Engineering Physics, IST, University of Lisbon

Lab 2: RC Circuit Analysis

Alexandre Sequeira (96503), Duarte Marques (96523), João Chaves (96540)

April 8, 2021

Contents

1	Introduction	1
2	Theoretical Analysis	2
2.1	Exercise 1	2
3	Simulation Analysis	3
3.1	Exercise 1	3
4	Conclusion	4

1 Introduction

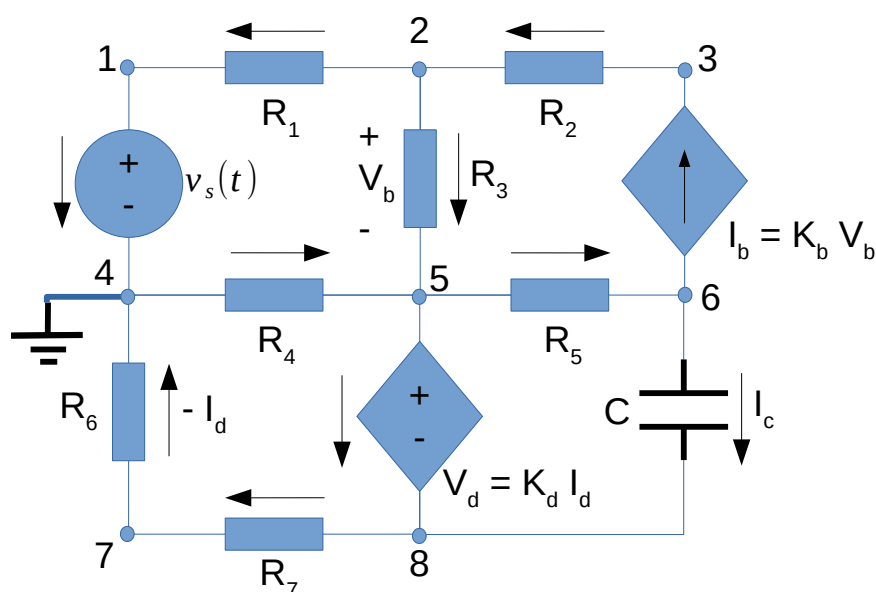


Figure 1: Circuit to be analysed in this laboratory assignment.

Designation	Value [V, kΩ, mS or μF]
R_1	1.04053890347
R_2	2.00185929606
R_3	3.06593231919
R_4	4.15163583349
R_5	3.03409481751
R_6	2.05654586148
R_7	1.00587575204
V_s	5.16821048288
C	1.0127707267
K_b	7.29055867767
K_d	8.22649929708

Table 1: Values obtained by running the file t2_datagen.py. Resistances R_i and constant K_d are in kΩ, voltage V_s is in volts, capacitance C is in microfarads and constant K_b is in milisiemens.

2 Theoretical Analysis

2.1 Exercise 1

In this section, the circuit shown in Figure 1 is analysed theoretically, by using the node method. The Kirchhoff Current Law (KCL) states that the sum of the currents converging or diverging in a node is null. The nodes considered for the following equations are those represented in Figure 1. Using KCL and Ohm's Law (which can also be written as $I = VG$) in nodes not connected to voltage sources and additional equations for nodes related by voltage sources, it is possible to obtain a linear system from which the voltages at nodes V_1 to V_8 and currents in resistances R_1 to R_7 can be determined.

The following linear system is obtained:

$$\begin{pmatrix}
 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_2} & 0 & -\frac{1}{R_3} & 0 & 0 & 0 \\
 0 & -K_b - \frac{1}{R_2} & \frac{1}{R_2} & 0 & K_b & 0 & 0 & 0 \\
 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\
 0 & -\frac{1}{R_3} & 0 & -\frac{1}{R_4} & \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} & -\frac{1}{R_5} & -\frac{1}{R_7} & \frac{1}{R_7} \\
 0 & K_b & 0 & 0 & -\frac{1}{R_5} - K_b & \frac{1}{R_5} & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & \frac{1}{R_6} + \frac{1}{R_7} & -\frac{1}{R_7} \\
 0 & 0 & 0 & -\frac{K_d}{R_6} & 1 & 0 & \frac{K_d}{R_6} & -1
 \end{pmatrix}
 \begin{pmatrix}
 V_1 \\
 V_2 \\
 V_3 \\
 V_4 \\
 V_5 \\
 V_6 \\
 V_7 \\
 V_8
 \end{pmatrix}
 =
 \begin{pmatrix}
 V_s \\
 0 \\
 0 \\
 0 \\
 0 \\
 0 \\
 0 \\
 0
 \end{pmatrix}
 \quad (1)$$

By solving the linear system 1, the following values for node voltages and branch currents (calculated by using Ohm's Law) are obtained:

Designation	Value [A or V]
I_1	-2.341433E-04
I_2	-2.451090E-04
I_3	-1.096569E-05
I_4	-1.194275E-03
I_5	-2.451090E-04
I_6	-9.601318E-04
I_7	-9.601318E-04
I_b	-2.451090E-04
I_c	4.336809E-19
I_{V_s}	-2.341433E-04
I_{V_d}	-9.601318E-04
V_1	5.168210E+00
V_2	4.924575E+00
V_3	4.433902E+00
V_5	4.958195E+00
V_6	5.701879E+00
V_7	-1.974555E+00
V_8	-2.940328E+00

Table 2: Values of node voltages (in volts) and branch currents (in amperes). Current I_i corresponds to the current passing through resistance R_i .

3 Simulation Analysis

3.1 Exercise 1

Table 3 shows the simulated operating point results for the circuit presented in Figure 1. Again, currents designated below as I_i refer to the currents passing through the respective resistances, R_i .

Designation	Value [A or V]
I_1	-2.34143e-04
I_2	-2.45109e-04
I_3	-1.09657e-05
I_4	-1.19428e-03
I_5	-2.45109e-04
I_6	-9.60132e-04
I_7	-9.60132e-04
I_b	-2.45109e-04
I_c	0.000000e+00
I_{V_s}	-2.34143e-04
I_{V_d}	-9.60132e-04
V_1	5.168210e+00
V_2	4.924575e+00
V_3	4.433902e+00
V_5	4.958195e+00
V_6	5.701879e+00
V_7	-1.97456e+00
V_8	-2.94033e+00

Table 3: Operating point analysis table. Currents I_i are in amperes; voltages V_i are in volts.

Comparing the theoretical analysis results presented in Table 2 and the results in Table 3, we can notice almost no differences. This was to be expected, since the circuit has no time dependency - meaning it's equal at any point in time. There is only a small difference between the two values of I_c , although it is negligible.

4 Conclusion