

# Circuits Theory and Electronic Fundamentals

Integrated Master in Engineering Physics, IST, University of Lisbon

## Lab 2: RC Circuit Analysis

Alexandre Sequeira (96503), Duarte Marques (96523), João Chaves (96540)

April 8, 2021

## Contents

<b>1</b>	<b>Introduction</b>	<b>1</b>
<b>2</b>	<b>Theoretical Analysis</b>	<b>2</b>
2.1	Exercise 1 . . . . .	2
<b>3</b>	<b>Simulation Analysis</b>	<b>3</b>
3.1	Exercise 1 . . . . .	3
3.2	Exercise 2 . . . . .	4
3.3	Exercise 3 . . . . .	5
3.4	Exercise 4 . . . . .	6
<b>4</b>	<b>Conclusion</b>	<b>8</b>

## 1 Introduction

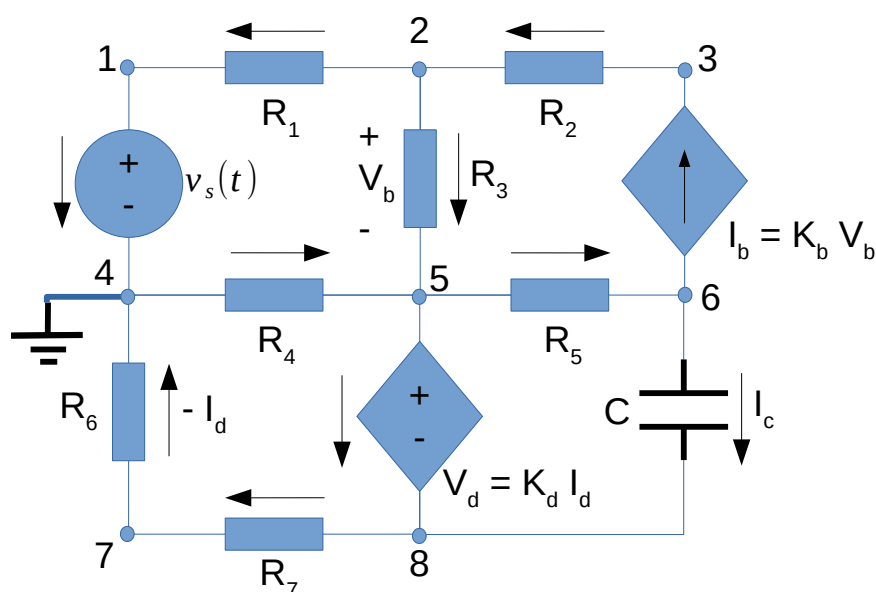


Figure 1: Circuit to be analysed in this laboratory assignment.

Designation	Value [V, kΩ, mS or μF]
$R_1$	1.04053890347
$R_2$	2.00185929606
$R_3$	3.06593231919
$R_4$	4.15163583349
$R_5$	3.03409481751
$R_6$	2.05654586148
$R_7$	1.00587575204
$V_s$	5.16821048288
$C$	1.0127707267
$K_b$	7.29055867767
$K_d$	8.22649929708

Table 1: Values obtained by running the file t2\_datagen.py. Resistances  $R_i$  and constant  $K_d$  are in kΩ, voltage  $V_s$  is in volts, capacitance  $C$  is in microfarads and constant  $K_b$  is in milisiemens.

## 2 Theoretical Analysis

### 2.1 Exercise 1

In this section, the circuit shown in Figure 1 is analysed theoretically, by using the node method. The Kirchhoff Current Law (KCL) states that the sum of the currents converging or diverging in a node is null. The nodes considered for the following equations are those represented in Figure 1. Using KCL and Ohm's Law (which can also be written as  $I = VG$ ) in nodes not connected to voltage sources and additional equations for nodes related by voltage sources, it is possible to obtain a linear system from which the voltages at nodes  $V_1$  to  $V_8$  and currents in resistances  $R_1$  to  $R_7$  can be determined.

The following linear system is obtained:

$$\begin{pmatrix}
 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_2} & 0 & -\frac{1}{R_3} & 0 & 0 & 0 \\
 0 & -K_b - \frac{1}{R_2} & \frac{1}{R_2} & 0 & K_b & 0 & 0 & 0 \\
 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\
 0 & -\frac{1}{R_3} & 0 & -\frac{1}{R_4} & \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} & -\frac{1}{R_5} & -\frac{1}{R_7} & \frac{1}{R_7} \\
 0 & K_b & 0 & 0 & -\frac{1}{R_5} - K_b & \frac{1}{R_5} & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & \frac{1}{R_6} + \frac{1}{R_7} & -\frac{1}{R_7} \\
 0 & 0 & 0 & -\frac{K_d}{R_6} & 1 & 0 & \frac{K_d}{R_6} & -1
 \end{pmatrix}
 \begin{pmatrix}
 V_1 \\
 V_2 \\
 V_3 \\
 V_4 \\
 V_5 \\
 V_6 \\
 V_7 \\
 V_8
 \end{pmatrix}
 =
 \begin{pmatrix}
 V_s \\
 0 \\
 0 \\
 0 \\
 0 \\
 0 \\
 0 \\
 0
 \end{pmatrix}
 \quad (1)$$

By solving the linear system 1, the following values for node voltages and branch currents (calculated by using Ohm's Law) are obtained:

Designation	Value [A or V]
$I_1$	-2.34143283E-04
$I_2$	-2.45108969E-04
$I_3$	-1.09656866E-05
$I_4$	-1.19427511E-03
$I_5$	-2.45108969E-04
$I_6$	-9.60131827E-04
$I_7$	-9.60131827E-04
$I_b$	-2.45108969E-04
$I_c$	4.33680869E-19
$I_{V_s}$	-2.34143283E-04
$I_{V_d}$	-9.60131827E-04
$V_1$	5.16821048E+00
$V_2$	4.92457529E+00
$V_3$	4.43390162E+00
$V_5$	4.95819534E+00
$V_6$	5.70187920E+00
$V_7$	-1.97455514E+00
$V_8$	-2.94032846E+00

Table 2: Values of node voltages (in volts) and branch currents (in amperes). Current  $I_i$  corresponds to the current passing through resistance  $R_i$ .

### 3 Simulation Analysis

#### 3.1 Exercise 1

Table 3 shows the simulated operating point results for the circuit presented in Figure 1. Again, currents designated below as  $I_i$  refer to the currents passing through the respective resistances,  $R_i$ .

Designation	Value [A or V]
$I_1$	-2.34143283e-04
$I_2$	-2.45108969e-04
$I_3$	-1.09656866e-05
$I_4$	-1.19427511e-03
$I_5$	-2.45108969e-04
$I_6$	-9.60131827e-04
$I_7$	-9.60131827e-04
$I_b$	-2.45108969e-04
$I_c$	0.00000000e+00
$I_{V_s}$	-2.34143283e-04
$I_{V_d}$	-9.60131827e-04
$V_1$	5.168210483e+00
$V_2$	4.924575288e+00
$V_3$	4.433901619e+00
$V_5$	4.958195341e+00
$V_6$	5.701879195e+00
$V_7$	-1.97455514e+00
$V_8$	-2.94032846e+00

Table 3: Operating point analysis table. Currents  $I_i$  are in amperes; voltages  $V_i$  are in volts.

Comparing the theoretical analysis results presented in Table 2 and the results in Table 3, we can notice almost no differences. This was to be expected, since the circuit has no time dependency - meaning it's equal at any point in time. There is only a small difference between the two values of  $I_c$ , although it is negligible.

### 3.2 Exercise 2

Designation	Value [A or V]
$I_1$	0.000000e+00
$I_2$	0.000000e+00
$I_3$	0.000000e+00
$I_4$	0.000000e+00
$I_5$	-2.84836e-03
$I_6$	0.000000e+00
$I_7$	0.000000e+00
$I_b$	0.000000e+00
$I_c$	-2.84836e-03
$I_{V_s}$	0.000000e+00
$I_{V_d}$	2.848364e-03
$V_1$	0.000000e+00
$V_2$	0.000000e+00
$V_3$	0.000000e+00
$V_5$	0.000000e+00
$V_6$	8.642208e+00
$V_7$	0.000000e+00
$V_8$	0.000000e+00

Table 4: Operating point analysis table. Currents  $I_i$  are in amperes; voltages  $V_i$  are in volts.

### 3.3 Exercise 3

Figure 2 shows the simulated transient analysis results obtained for the voltage in node 6.

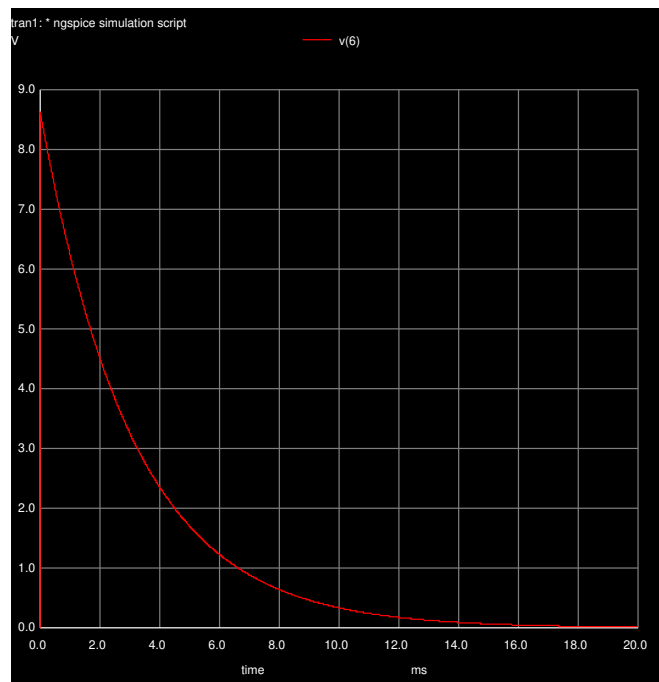


Figure 2: Value of  $v_6(t)$  in the time interval  $[0,20]$  ms.

### 3.4 Exercise 4

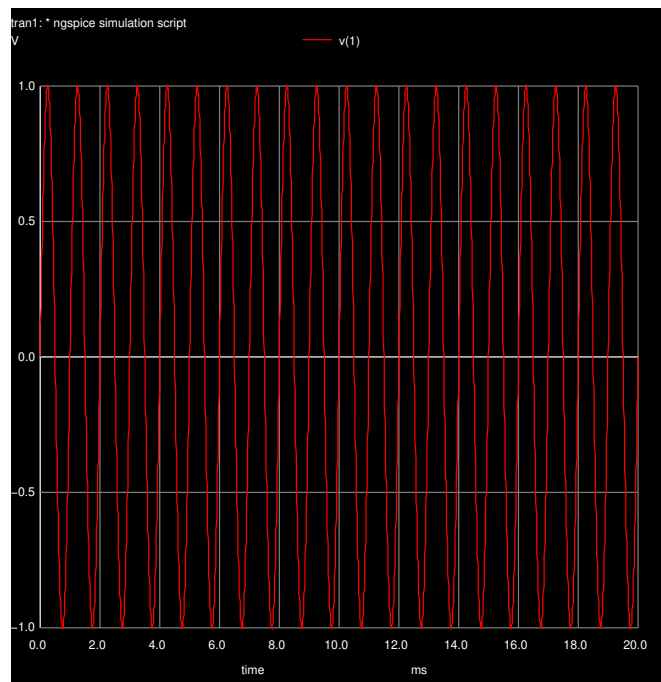


Figure 3: Stimulus voltage in time interval [0,20] ms.

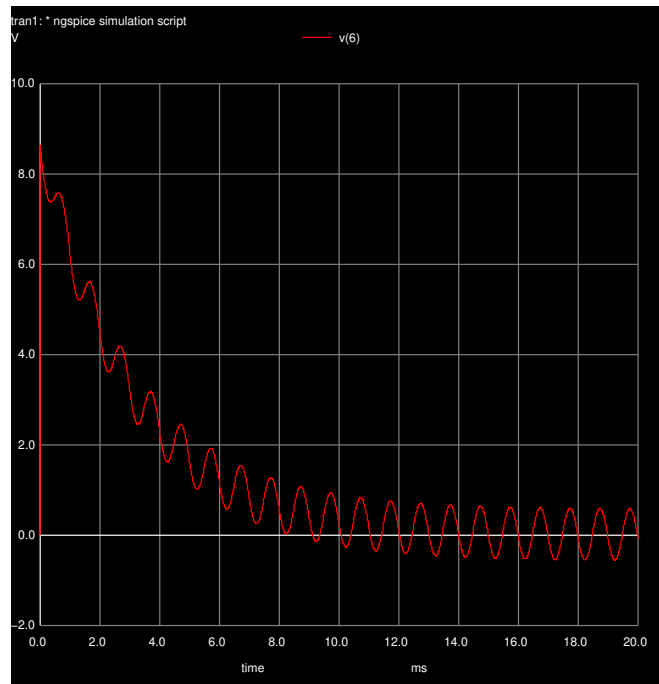


Figure 4: Forced response on node 6 in time interval [0,20] ms.

## 4 Conclusion

Theoretical		Simulation	
Designation	Value [A or V]	Designation	Value [A or V]
$I_1$	-2.34143283E-04	$I_1$	-2.34143283e-04
$I_2$	-2.45108969E-04	$I_2$	-2.45108969e-04
$I_3$	-1.09656866E-05	$I_3$	-1.09656866e-05
$I_4$	-1.19427511E-03	$I_4$	-1.19427511e-03
$I_5$	-2.45108969E-04	$I_5$	-2.45108969e-04
$I_6$	-9.60131827E-04	$I_6$	-9.60131827e-04
$I_7$	-9.60131827E-04	$I_7$	-9.60131827e-04
$I_b$	-2.45108969E-04	$I_b$	-2.45108969e-04
$I_c$	4.33680869E-19	$I_c$	0.000000000e+00
$I_{V_s}$	-2.34143283E-04	$I_{V_s}$	-2.34143283e-04
$I_{V_d}$	-9.60131827E-04	$I_{V_d}$	-9.60131827e-04
$V_1$	5.16821048E+00	$V_1$	5.168210483e+00
$V_2$	4.92457529E+00	$V_2$	4.924575288e+00
$V_3$	4.43390162E+00	$V_3$	4.433901619e+00
$V_5$	4.95819534E+00	$V_5$	4.958195341e+00
$V_6$	5.70187920E+00	$V_6$	5.701879195e+00
$V_7$	-1.97455514E+00	$V_7$	-1.97455514e+00
$V_8$	-2.94032846E+00	$V_8$	-2.94032846e+00

Table 5: Exercise 1 comparison.