

# Circuit Theory and Electronics Fundamentals

Integrated Master in Engineering Physics, IST, University of Lisbon

Lab 1: Circuit analysis methods

March 25, 2021

## Contents

|          |                                    |          |
|----------|------------------------------------|----------|
| <b>1</b> | <b>Introduction</b>                | <b>1</b> |
| <b>2</b> | <b>Theoretical Analysis</b>        | <b>2</b> |
| <b>3</b> | <b>Time response</b>               | <b>2</b> |
| <b>4</b> | <b>Frequency response</b>          | <b>3</b> |
| <b>5</b> | <b>Simulation Analysis</b>         | <b>3</b> |
| 5.1      | Operating Point Analysis . . . . . | 3        |
| 5.2      | Transient Analysis . . . . .       | 4        |
| 5.3      | Frequency Analysis . . . . .       | 5        |
| 5.3.1    | Magnitude Response . . . . .       | 5        |
| 5.3.2    | Phase Response . . . . .           | 6        |
| 5.3.3    | Input Impedance . . . . .          | 7        |
| <b>6</b> | <b>Conclusion</b>                  | <b>8</b> |

## 1 Introduction

The objective of this laboratory assignment is to study a circuit containing a sinusoidal voltage source  $V_I$  connected to a resistor  $R$  and a capacitor  $C$  in series. The circuit can be seen in Figure 1.

In Section 2, a theoretical analysis of the circuit is presented. In Section 5, the circuit is analysed by simulation, and the results are compared to the theoretical results obtained in Section 2. The conclusions of this study are outlined in Section 6.

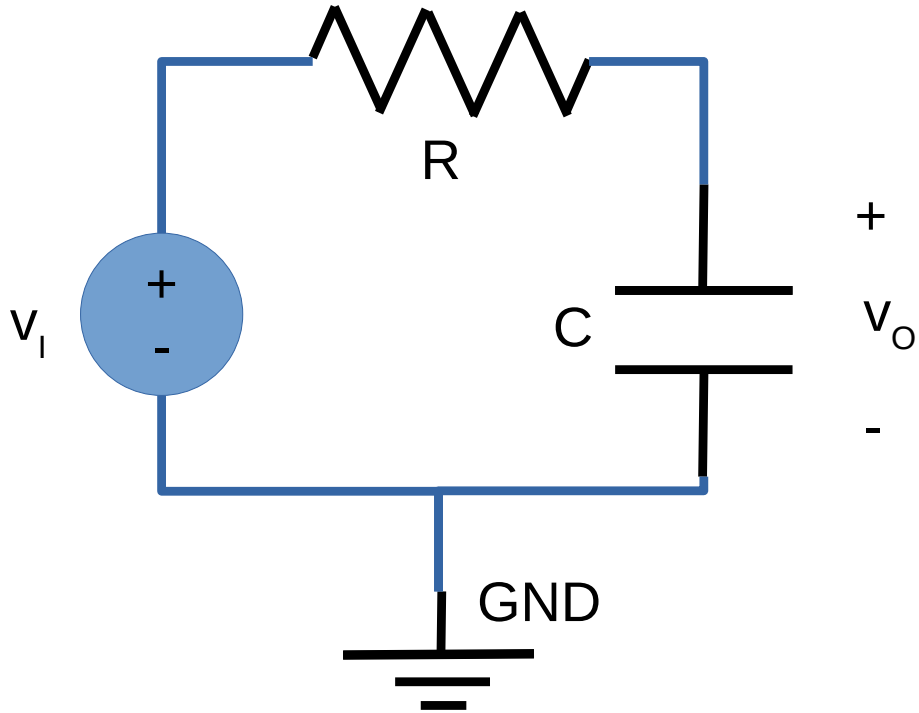


Figure 1: Voltage driven serial RC circuit.

## 2 Theoretical Analysis

In this section, the circuit shown in Figure 1 is analysed theoretically, in terms of its time and frequency responses.

## 3 Time response

The circuit consists of a single V-R-C loop where a current  $i(t)$  circulates. The voltage source  $v_I(t)$  drives its input, and the output voltage  $v_O(t)$  is taken from the capacitor terminals. Applying the Kirchhoff Voltage Law (KVL), a single equation for the single loop in the circuit can be written as

$$Ri(t) + v_O(t) = v_I(t). \quad (1)$$

Because  $v_O$  is the voltage between capacitor C's plates, it is related to the current  $i$  by

$$i(t) = C \frac{dv_O}{dt}. \quad (2)$$

Hence, Equation (1) can be rewritten as

$$RC \frac{dv_O}{dt} + v_O(t) = v_I. \quad (3)$$

Equation (3) is a linear differential equation whose solution is a superposition of a natural solution  $v_{On}$  and a forced solution  $v_{Of}$ :

$$v_O(t) = v_{On}(t) + v_{Of}(t). \quad (4)$$

As learned in the theory classes the natural solution is of the form

$$v_{On}(t) = Ae^{-\frac{t}{RC}}, \quad (5)$$

where  $A$  is an integration constant.

The forced solution is of the form given in Equation (6) and is illustrated in Figure 2.

$$V_{Of}(t) = |\bar{V}_{Of}| \cos(\omega t + \angle \bar{V}_{Of}), \quad (6)$$

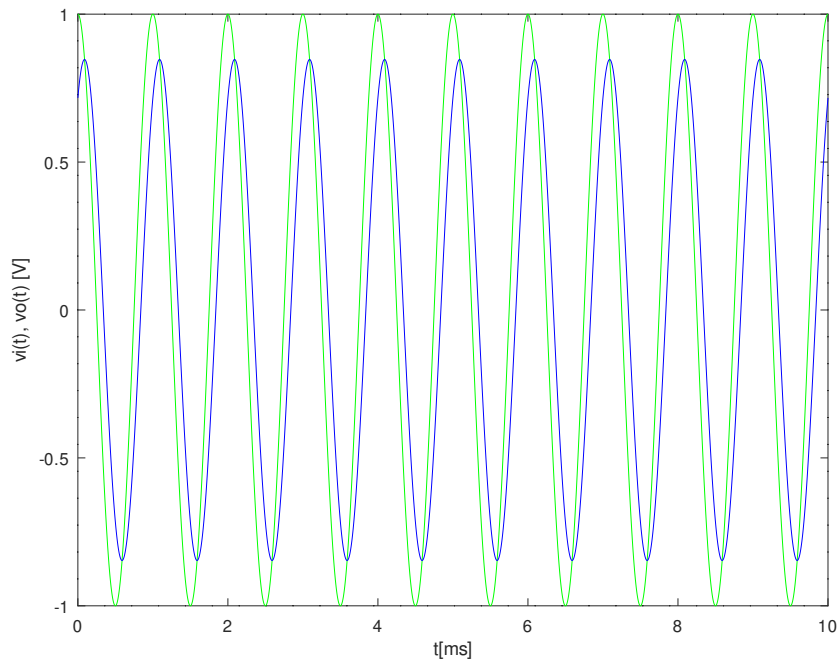


Figure 2: Forced sinusoidal response.

## 4 Frequency response

This section has no text. Wait... Now it has!

## 5 Simulation Analysis

### 5.1 Operating Point Analysis

Table 1 shows the simulated operating point results for the circuit under analysis. Compared to the theoretical analysis results, one notices the following differences: describe and explain the differences.

| Name    | Value [A or V] |
|---------|----------------|
| @cb[i]  | 0.000000e+00   |
| @ce[i]  | 0.000000e+00   |
| @q1[ib] | 7.022567e-05   |
| @q1[ic] | 1.404513e-02   |
| @q1[ie] | -1.41154e-02   |
| @q1[is] | 5.765392e-12   |
| @rc[i]  | 1.411536e-02   |
| @re[i]  | 1.411536e-02   |
| @rf[i]  | 7.022567e-05   |
| @rs[i]  | 0.000000e+00   |
| v(1)    | 0.000000e+00   |
| v(2)    | 0.000000e+00   |
| base    | 2.254108e+00   |
| coll    | 5.765392e+00   |
| emit    | 1.411536e+00   |
| vcc     | 1.000000e+01   |

Table 1: Operating point. A variable preceded by @ is of type *current* and expressed in Ampere; other variables are of type *voltage* and expressed in Volt.

## 5.2 Transient Analysis

Figure 3 shows the simulated transient analysis results for the circuit under analysis. Compared to the theoretical analysis results, one notices the following differences: describe and explain the differences.



Figure 3: Transient output voltage

## 5.3 Frequency Analysis

### 5.3.1 Magnitude Response

Figure 4 shows the magnitude of the frequency response for the circuit under analysis. Compared to the theoretical analysis results, one notices the following differences: describe and explain the differences.



Figure 4: Magnitude response

### 5.3.2 Phase Response

Figure 5 shows the magnitude of the frequency response for the circuit under analysis. Compared to the theoretical analysis results, one notices the following differences: describe and explain the differences.



Figure 5: Phase response

### 5.3.3 Input Impedance

Figure 6 shows the magnitude of the frequency response for the circuit under analysis. Compared to the theoretical analysis results, one notices the following differences: describe and explain the differences.

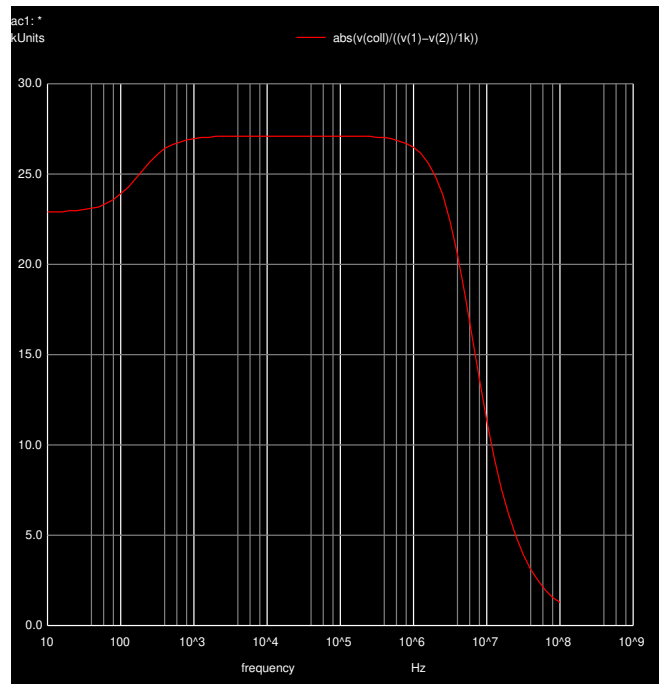


Figure 6: Input impedance

## 6 Conclusion

In this laboratory assignment the objective of analysing an RC circuit has been achieved. Static, time and frequency analyses have been performed both theoretically using the Octave maths tool and by circuit simulation using the Ngspice tool. The simulation results matched the theoretical results precisely. The reason for this perfect match is the fact that this is a straightforward circuit containing only linear components, so the theoretical and simulation models cannot differ. For more complex components, the theoretical and simulation models could differ but this is not the case in this work.